



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents—printed and online—are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.


For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Aug 1946

Title: Frequency Meters as Master Oscillators

Author: Commander E.H. Conklin, W3JUX

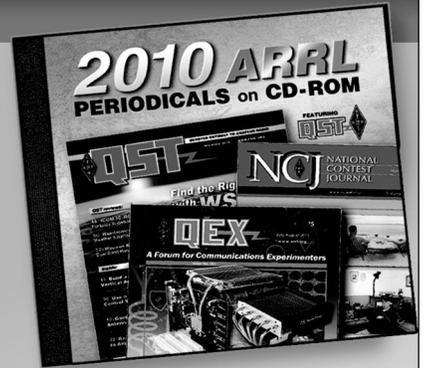[Click Here to Report a Problem with this File](#)



2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001

Only \$24.95*

*plus shipping and handling

Additional sets available:

2009 Ed., ARRL Order No. 1486, \$24.95
 2008 Ed., ARRL Order No. 9406, \$24.95
 2007 Ed., ARRL Order No. 1204, \$19.95
 2006 Ed., ARRL Order No. 9841, \$19.95
 2005 Ed., ARRL Order No. 9574, \$19.95
 2004 Ed., ARRL Order No. 9396, \$19.95
 2003 Ed., ARRL Order No. 9124, \$19.95
 2002 Ed., ARRL Order No. 8802, \$19.95
 2001 Ed., ARRL Order No. 8632, \$19.95



ARRL The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.
 ONLINE WWW.ARRL.ORG/SHOP
 ORDER TOLL-FREE 888/277-5289 (US)

Frequency Meters as Master Oscillators

An Easily-Constructed Amplifier for Use with Surplus Units

BY COMMANDER E. H. CONKLIN,* USNR, W3JUX

THERE is an old saying that if you want a really good frequency standard—oscillator or crystal—don't make it drive a transmitter, too. This saying has its value, to be sure, but from time to time new developments make it possible to get some usable power out of a frequency standard. For example, many Navy-transmitter master oscillators perform every bit as well as many crystal stages, once set on the right frequency, and the Navy's best shipboard frequency meter—Model LR—produces several watts of power.

A less-complicated frequency meter, the Navy's Model LM series and the Army's Type SCR-211, has occasionally served as a master oscillator by driving an amplifier with its normal output. This model has already appeared in the surplus market at a price around \$20 (without calibration). The meter is being handled by Hoffman Radio Corp., 1601 East 16th Street, Los Angeles 25, California, and by Hallcrafters in Chicago, as agents for the RFC, at somewhat higher prices (subject to service discounts), but comes complete with instructions and book of individually-calibrated dial settings.¹ Large quantities appear in the Navy's allowances of radio material for Naval Reserve members. It has a crystal-controlled calibrator oscillator to provide check-points, and a tunable oscillator with tone modulator to interpolate

*Conklin Radio Co., 6800 Clarendon Road, Bethesda 14, Md.

¹According to information at the time of writing. Changes in the surplus picture may modify these prices considerably.


between check-points, all built into a nice unit approximately 8-inches cube, weighing 11½ pounds.

Some of these units are operated from an aircraft power supply, while others are mounted in a battery case or are provided with a 110-volt a.c. power supply. In the absence of the latter, it is necessary to provide only ¾ ampere at 12-volts a.c. or d.c. for the heaters and 10 ma. at 180 to 475 volts for the plates—the first readily obtainable from a small filament transformer and the second from a receiver. If the less-expensive meter without the power supply is purchased, Type CQC-20104A power units can be obtained separately at only \$7.50 as Item G2F-1 on the surplus list of Communications Measurements Laboratory, 120 Greenwich Street, New York 6, New York.¹

The tunable oscillator uses a Type 77 tube, the crystal oscillator and harmonic generator uses a 6A7, and the tone modulator a 76. The 2000-4000-kc. output for driving an external amplifier is taken from the arm of a potentiometer connected between the tunable-oscillator plate blocking condenser and ground.

A Choke-Coupled Amplifier

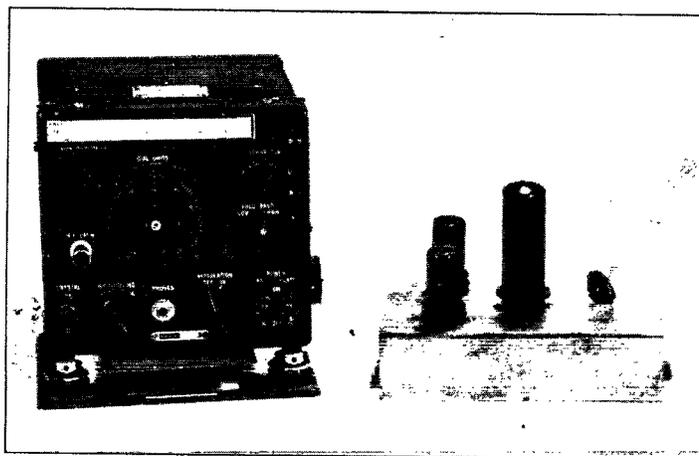An amplifier that will permit controlling a transmitter from the output of the frequency meter, based on a circuit furnished by Lt. Col. Byron E. Hargrove, W9LFU (who spent his Army career in the Bureau of Ships, Navy Department, after leaving the Signal Corps labora-



The amplifier described in the text alongside the Model LM frequency meter which drives it. It is built on a chassis 8 inches wide, 4 inches deep, and 2 inches high. Parts layout is not critical, since only the last stage operates as a tuned amplifier.

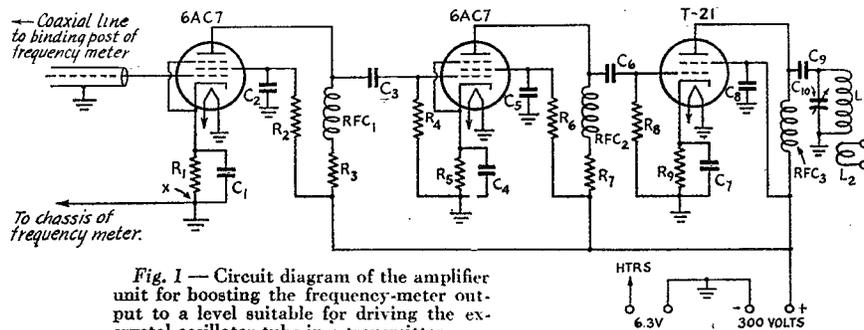


Fig. 1 — Circuit diagram of the amplifier unit for boosting the frequency-meter output to a level suitable for driving the external crystal-oscillator tube in a transmitter.

C₁ to C₉, inc. — 500- to 1000- μ fd. ceramic, 600 volts.
 C₁₀ — 100- μ fd. variable.
 R₁, R₅ — 300 ohms, 2 watts.
 R₂, R₆ — 60,000 ohms, 2 watts.
 R₃, R₇ — 1000 ohms (or higher), 2 watts.
 R₄, R₈ — 0.1 megohm, 1/2 watt.
 R₉ — 500 ohms, 2 watts.

L₁, L₂ — 3.5-Mc. coil with link, such as a junior transmitting coil or receiver-type plug-in coil. Suitable dimensions for a 1 1/4-inch diameter coil form are 50 turns of No. 22 enameled, closewound, for L₁, and 5 or more turns of the same wire for L₂.
 RFC₁, RFC₂, RFC₃ — 2.5-mh. r.f. choke.

tories at Fort Monmouth) is shown in the photograph. The wiring diagram differs from Lt. Col. Hargrove's circuit chiefly in the use of r.f. chokes instead of simple resistance coupling in the plate circuits of the two 6AC7 amplifiers. The Taylor T-21 output stage is used on the 3.5-4.0-Mc. band, although it could operate at 1.7-2.0 Mc. as well. The latter range will be preferred where it is intended to drive an existing 3.5-Mc. crystal stage as an unneutralized doubler.

For break-in, the key should be connected between the bottom of R₁ and ground (point "X" on schematic), opening the d.c. cathode circuit of the first 6AC7. The coaxial cable from the frequency meter to the first amplifier tube is desirable to reduce radiation which might be picked up by the station receiver when operating break-in on the transmitter frequency. However, its capacity by-passes some of the r.f. input to the first amplifier and, therefore, it should be kept reasonably short. If the shielded coax is omitted, a common ground should connect the frequency meter and the amplifier in order to provide an r.f. return.

The resistor and capacitor values were found to be not at all critical. Inasmuch as no grid current flows in the grid leaks of the second and third stages when plate and screen voltages are applied and when cathode-bias resistors are used, the grid-leak values are selected purely to avoid loss of r.f. and not for operating bias. Grid chokes in series with them were found to cause a modest improvement in gain, as measured by the grid current of the next stage when no plate and screen voltages are applied to it, but not enough to justify their cost. So long as the grid-leak resistors are not by-passed, the use of grid chokes does not increase the tendency for the amplifier to oscillate at a parasitic frequency as a tuned-plate tuned-grid oscillator, with the chokes form-

ing the inductances.

The by-pass and coupling condensers used are actually 680- μ fd. axial-lead ceramic capacitors, plus or minus 180 μ fd., which are available for a few cents from a mail-order radio supply house. They are shorter than a 1/2-watt resistor and can be mounted directly on the socket terminals in an extremely-compact arrangement with very short leads. The reactance of a by-pass circuit is probably less with these condensers than it is with common 0.1- μ fd. paper by-pass condensers which cost several times as much.

The use of radio-frequency chokes instead of plate resistors increased the stage gain very much — at least a third — without losing any plate voltage in the resistors which otherwise would happen. With Type 6AC7 tubes in the first two stages, there was no tendency toward oscillation in the second and third stages through the r.f. chokes but later, when trying other types of tubes, this form of oscillation occurred. It is deemed to be desirable, therefore, to insert resistors of 1000 ohms or more in series with the chokes. These resistors are in series with the tuned circuits of the parasitic oscillations through the chokes and, therefore, suppress the tendency completely.


Link-coupled output is used, although normally it will be more convenient to locate the amplifier reasonably close to the former crystal-oscillator stage of the transmitter and to feed the latter capacitively, operating the stage as a doubler unless it is a pentode or tetrode, with no tendency toward oscillation when worked straight through as an amplifier.

A voltage of only 300 was used on this unit, although it is recognized that a higher voltage may be used, with adjustment of the screen and plate resistors to the necessary higher values. It will then be necessary also to increase the cathode

(Continued on page 150)

TYPE--750
Overload Relay

with Electrical
Reset

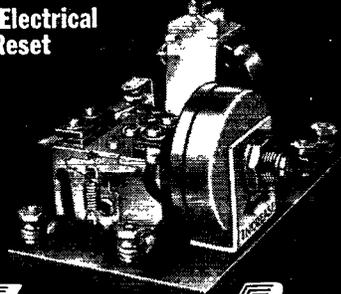

Advance Relays

The Advance type "750" relay is designed for accurate and positive protection against current surges and continuous overloads. Safeguard your expensive power tubes in radio transmitters.

Type 750 overload relay is supplied in either of two groups: type A, which allows the relay to open the contact circuit on any current value between 250 and 500 mills, and, type B for any setting between 500 and 1000 mills. Both types supplied as DPST with 1/4" pure silver contacts and 110 v. A.C. (or specified voltage) reset coil.

A manual reset relay (Type 700) of similar characteristics is also available.

Amateur Net Price (At Your Jobber) —
Type 750A or 750B... \$7.92
Type 700A or 700B... \$6.10

Advance Relay Catalog free on request.

 **ADVANCE**
ELECTRIC & RELAY CO.
1260 West 2nd Street
Los Angeles 26, Calif., U. S. A.
Phone Michigan 9331

Now • QUICK SERVICE

ON

HALLICRAFTERS • NATIONAL • RME • HOWARD
ALIGNMENT and REPAIRS

CML Service Laboratory will check sensitivity, signal to noise ratio, and selectivity, with laboratory standard test equipment, to insure maximum performance.

Factory Service Division

COMMUNICATION MEASUREMENTS LABORATORY
120 GREENWICH STREET NEW YORK 6

Frequency Meters as Oscillators

(Continued from page 35)

resistor in the final amplifier to provide the bias voltage necessary to hold the plate current of this tube within its rating.

At 300 volts, a 6V6 produces nearly as much output as a T-21 or 6L6, but the latter are to be preferred for higher plate voltages. Triodes and tetrodes were also tried in the untuned stages, with good results but with reduced voltage gain. The 6V6 and 6J5 required an increase of the cathode resistor to 500 ohms to hold the plate current within the ratings. It is evident that this amplifier can be built up from almost any triode, tetrode, or pentode tubes that are on hand and which have fair power-handling ability.

Operation

The presence of the r.f. amplifier attached to the output of the frequency meter does not in any way detract from the value of the latter for its originally-intended purpose. Whether used as such or to drive the transmitter, the operating procedure is the same although, with well-shielded leads, it is necessary to clip a wire on to the frequency-meter output or even to couple it to the receiving antenna, to check the frequency of an incoming signal.

After the frequency meter has warmed up, the dial on the tunable oscillator should be set at the nearest check-point. The crystal oscillator in the meter is then turned on, and the "corrector" is adjusted until the tunable oscillator is in zero beat with a harmonic of the crystal frequency which provides the check-point, while listening with headphones that are plugged into the frequency-meter 'phone jack. If low audio beat frequencies cannot be heard, the exact dial setting of zero beat can be estimated with satisfactory accuracy by noting the dial settings on each side which produce the same low-frequency audio tone, the midpoint of these two settings being used. The crystal oscillator is then turned off, and the tunable-oscillator dial is returned to the desired setting between check-points.

The accuracy of this type of frequency meter depends upon the accuracy of the crystal oscillator and its harmonics which serve as check-points, and upon the ability of the tunable oscillator to retain a calibration between the check-points. Under severe changes of temperature, humidity, tubes and so on, the cumulative error should be well within 0.01 per cent at any point, which is 100 cycles per megacycle. It should be very much better at the check-points, which generally fall at the edges of the amateur bands. In practice, the errors will be compensating to some extent, so that a frequency can be determined within a few hundred cycles. The tunable oscillator was not built to maintain this accuracy under large temperature or humidity changes, while warming up, or for long periods of time, without being

(Continued on page 132)



De Luxe
SPEED KEY

Model
CP 810

Amateur
Net Price
\$9.75

One of the finest commercial or amateur bugs available. Chrome finished base and super-structure. Springs made of selected blue spring steel for uniform performance in all keys. Nine points of adjustment to suit the most critical touch. Fully adjustable. Silver contacts 3/16" diameter.


MODEL CP 510 SPEED KEY • Similar to above except the base is Battleship gray wrinkle finish. Amateur Net Price \$6.75.

TELEGRAPH
Apparatus Co.

412 SOUTH GREEN ST.

CHICAGO 7, ILLINOIS

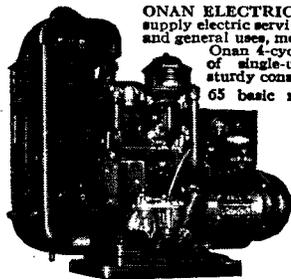ELECTRICITY
FOR RADIO AND ELECTRONIC APPLICATIONS



ONAN ELECTRIC GENERATING PLANTS supply electric service for electronics applications and general uses, mobile or stationary. Driven by Onan 4-cycle gasoline engines, they are of single-unit, compact design and sturdy construction.

65 basic models ranging in capacity from 550 to 35,000 watts. Standard A.C. models, 115-volt, 60-cycle, single-phase. Standard D.C. models, 32 to 115 volts. Special voltages to 660 A.C., and 6 to 4000 volts D.C. 5 KW to 35 KW units available in 3-phase. High frequencies to 800 cycles. Combination A.C.-D.C. types. Write for detailed literature or engineering assistance.

D. W. ONAN & SONS 2438 Royalston Ave. Minneapolis 5, Minn

Mass. Radio School

271 Huntington Ave., Boston 15, Mass.

For over 27 years the educational radio center of New England. Prepares for all U. S. Government Radio Operators' Licenses. Also gives Radio Technician Training. Approved courses for Veteran Training under G.I. Bill.

Licensed by Commonwealth of Mass.,
Department of Education

(Continued from page 130)

rechecked against the crystal harmonics and, therefore, it falls short of the performance of the best Navy-transmitter master oscillators. However, it will compare very favorably with almost any similar piece of equipment constructed by amateurs at a similar cost, and at much more trouble.

About the Author

• Commander Elmer H. "Bill" Conklin, W3JUX, admits his best claim to fame is being the husband of W9SLG/3! That is, when he isn't devoting his time to conducting u.h.f. columns for magazines such as the prewar *Radio*, working on the development of u.h.f. antennas, talking 44 miles on crystal-controlled 'phone on frequencies above 5000 Mc., or serving in the Fleet Technical Section, Chief of Naval Communications, Navy Dept., Washington, D. C. A graduate of Northwestern University with a B.S. degree, "Bill" has been licensed since 1922, his first call being W9DBF. He holds WAC and RCC certificates.

Happenings

(Continued from page 40)

tunity for members to put their representation in the hands of a member of their own choosing. Full Members are urged to take the initiative and file nominating petitions immediately.

For the Board of Directors:

K. B. WARNER,
Secretary

June 1, 1946

Propagation Predictions

(Continued from page 46)

9 of the article are from the report IRPL-D15. The charts in the article by E. H. Conklin in January, *QST*, "The Bright New World — of Sunspots," are also from IRPL reports.

The CRPL hopes that in making available to the general public the radio wave propagation information and techniques which were so widely and so successfully used by the Army and Navy during the war, the radio amateur's understanding of propagation conditions and his enjoyment of the time he is on the air will be significantly increased.

Strays

"KC," writing in *APCO Bulletin*, says "A short time ago I heard one station ask: 'WX?,' and the queried station cracked back: 'It's dark here.'"